

Symbols Of Parts Of An Electrical Circuit

Look at the symbols given in the first column. Write the name of the part in the second column, use a pencil to draw the symbol in the third column, and based on what you have read, describe the role of each component in the last column.

Symbol	Name of the part	Symbol	Purpose and use of this part in a circuit
			
			
			
			
			
			
			
			